

M.Sc. PHYSICS
 SECOND SEMESTER
 ELECTRONICS
 MSP - 203

**SET
 A**

[USE OMR FOR OBJECTIVE PART]

Duration: 1:30 hrs.

Full Marks: 35

(Objective)





Time: 15 mins.

Marks: 10


1 × 10 = 10

Choose the correct answer from the following:

    1. Identify the correct output waveform of the circuit shown below (assume the diode to be ideal)



 2. The magnitude of the output voltage for the circuit given below is _____ Volts.



- a. 0.35
 c. 0.45

- b. 0.55
 d. 0.65

3. A Zener diode when biased correctly
 - a. Never overheats
 - b. Acts as a fixed resistance
 - c. Has a constant voltage across it
 - d. Has a constant current across it
4. When the differential amplifier is operated single-ended, _____
 - a. the output is grounded
 - b. one input is grounded and signal is applied to other
 - c. both inputs are connected together
 - d. the output is not inverted
5. A certain inverting amplifier has R_i of 1 k Ω and R_f of 100 k Ω . The closed-loop voltage gain is _____
 - a. 100,000
 - b. 1000
 - c. 100
 - d. 101
6. In a comparator, if we get input as $A > B$ then the output will be _____
 - a. 1
 - b. 0
 - c. A
 - d. B
7. Which combinational circuit is renowned for selecting a single input from multiple inputs & directing the binary information to output line?
 - a. Data Selector
 - b. Data distributor
 - c. Both data selector and data distributor
 - d. DeMultiplexer
8. The truth table for an S-R flip-flop has how many VALID entries?
 - a. 1
 - b. 2
 - c. 3
 - d. 4
9. What is one disadvantage of an S-R flip-flop?
 - a. It has no Enable input
 - b. It has a RACE condition
 - c. It has no clock input
 - d. Invalid State
10. A J-K flip-flop can be obtained from the clocked S-R flip-flop by augmenting _____
 - a. Two AND gates
 - b. Two NAND gates
 - c. Two NOT gates
 - d. Two OR gates

-- --- -


(Descriptive)

Time : 1 hr. 15 mins.


Marks: 25

[Answer question no.1 & any two (2) from the rest]

 1. Determine V_o , I_I , I_{D1} and I_{D2} for the parallel diode configuration shown in figure below. 5




 2. a. Show that the output function of the circuit shown below is $f = \sum m(1, 2, 4, 6)$ 5+5=10



- b. Implement $F(A, B, C, D) = \sum m(1,3,4,11,12,13,14, 15)$ using 8×1 MUX.
3. a. What do you understand by transistor biasing? What is its need? 2+8=10
- b. Describe the potential divider method of transistor biasing in detail. How stabilization of operating point is achieved by this method?

 4. a. Discuss the operation of Op-Amp as integrator and differentiator. 6+4=10
- b. A three-stage Op-Amp circuit shown below is used to provide voltage gains of +10, -18 and -27. Find the values of R_1 , R_2 , R_3 and V_{out} . Use a $270\text{ k}\Omega$ feedback resistor for all the stages and input voltage of $150\text{ }\mu\text{V}$.



5. a. Draw the logic diagram and explain the operation of a Clocked JK Flip Flop for all possible combination of J and K. 4+4+2
=10
- b. Draw the truth table, characteristics table, excitation table and state transition diagram for JK Flip Flop.
- c. What is race around condition in JK flip-flop? Write the methods to avoid such condition.

== *** ==